

# PHASE I - BEFORE EXPERIMENTATION


## PART 1

**\*Obrigatório**

1. Endereço de email \*

---

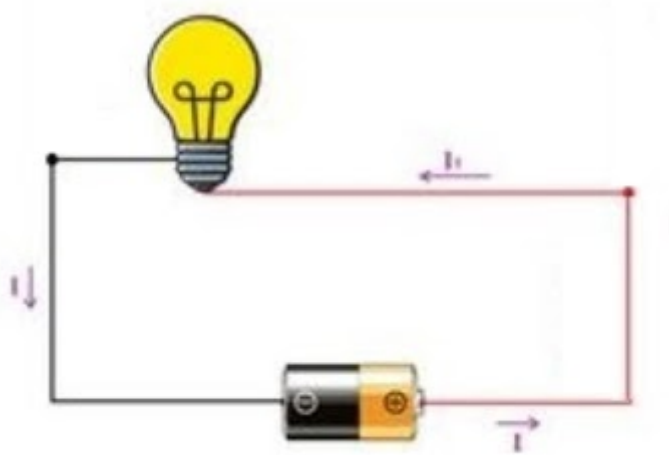2. Como fazer acender uma lâmpada? Penso que ... \*



*Marcar apenas uma oval.*

- you connect the positive pole of the battery to the light bulb with a conductive wire.
- components are connected in a closed circuit.
- the negative pole of the battery is connected to the light bulb with a conductive wire
- none of the above.

3. The light bulb turns on in ... \*



A



B



C



D

Marcar apenas uma oval.


A

B

C

D

4. The light bulb turns on in ... \*

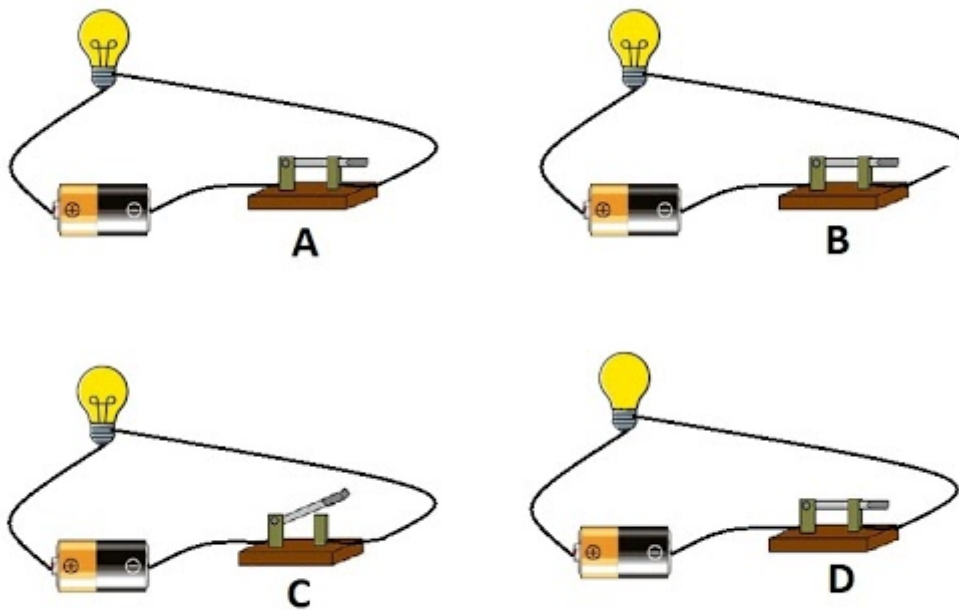

Marcar apenas uma oval.

- A
- B
- C
- D

---

Este conteúdo não foi criado nem aprovado pela Google.

Google Formulários